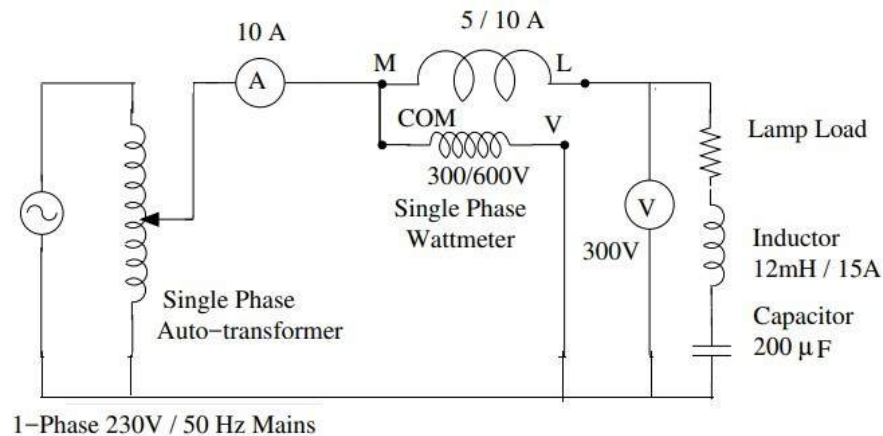


Measurement of Power in R-L-C series circuit

CIRCUIT DIAGRAM:**OBSERVATION TABLE:**

Sr. No.	V_s (V)	I_s (A)	V_R (V)	V_{coil} (V)	V_C (V)	Active Power (P) (Watts)
1	230.1V	1.54A	229.7V	6.23V	24.86V	353.4W
2	230.1V	3.05A	224.7V	12.7V	48.8V	693.3W
3	230.1V	3.81A	223.2	15.69V	60.8V	858.3W

CALCULATIONS:**Useful formulae:**

$$\text{Apparent power } S = V_s \cdot I_s$$

$$\text{Power Factor} = P / S$$

$$\text{Total circuit impedance } Z_s = V_s / I_s$$


$$\text{Coil impedance } Z_{coil} = V_{coil} / I_s$$

$$\text{Resistance of Lamp load } R = V_R / I_s$$

$$\text{Capacitive reactance } X_C = V_C / I_s$$

The parameters of the circuit can be obtained by solving following two equations:

$$Z_s^2 = (R+r)^2 + (X_L - X_C)^2 \text{ and } Z_{coil}^2 = r^2 + X_L^2$$

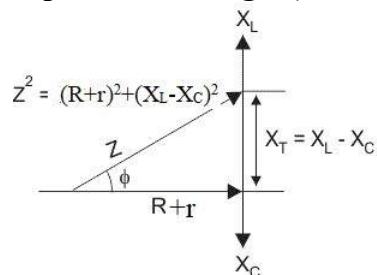Impedance Triangle (For $X_L > X_C$)

	Sr No.	V_s (V)	I_s (A)	V_R (V)	V_{coil} (V)	V_c (V)	(P) watt
(2 bulbs)	1	230.1	1.54	229.7	6.23	24.86	359.4
4 bulbs	2	230.1	3.05	224.7	12.7	41.8	693.3
5	3	230.1	3.81	223.2	15.67	60.8	858.3

1800
9/7/22

Calculations :-

- For (2 bulbs) $V_s = 230.1V$; $I_s = 1.54A$
- 1) Apparent power $S = V_s \times I_s = 354.354 VA$
- 2) Power factor $P/S = \cos \phi = 0.997$
- 3) Total circuit Impedance $Z_s = V_s / I_s = 149.415 \Omega$
- 4) Coil Impedance $Z_{coil} = \frac{V_{coil}}{I_s} = 4.045 \Omega$
- 5) Resistance of lamp load $= R = V_R / I_s = 149.155 \Omega$
- 6) Capacitive Reactance $X_c = V_c / I_s = 16.14 \Omega$
- $C = \frac{1}{\omega X_c} = 197.2 \mu F$

$$X_L = ? \quad \tau = ?$$

$$Z_s^2 = (R + \tau)^2 + (X_L - X_c)^2 \quad \text{and} \quad Z_{coil}^2 = r^2 + X_L^2 \quad \text{--- (i)}$$

solving (i) & (ii) simultaneously,

$$Z_s^2 = (R + \sqrt{Z_{coil}^2 - X_L^2})^2 + (X_L - X_c)^2$$

$$Z_s^2 = R^2 + 2R\sqrt{Z_{coil}^2 - X_L^2} + Z_{coil}^2 - X_L^2 + X_L^2 - 2X_L X_c + X_c^2$$

$$Z_s^2 = R^2 + 2R\sqrt{Z_{coil}^2 - X_L^2} + Z_{coil}^2 - 2X_L X_c + X_c^2$$

$$22324.84 = 22247.214 + 16.36 - 32.28X_L + 260.50 + 298.31(\sqrt{16.36 - X_L^2})$$

$$-199.233 = -32.28X_L + 298.31(\sqrt{16.36 - X_L^2})$$

$$32.28X_L - 199.233 = 298.31(\sqrt{16.36 - X_L^2})$$

$$1041.99X_L^2 - 12862.48X_L + 39693.79 = 88988.86(16.36 - X_L^2)$$

$$1041.99X_L^2 - 12862.48X_L + 39693.79 = 1455857.75 - 88988.86X_L^2$$

$$90036.85X_L^2 - 12862.48X_L + 1416163.96 = 0$$

$$90036.85X_L^2 - 12862.48X_L - 1416163.96 = 0$$

$$X_L = 4.038 \Omega \quad X_L = -3.895 \Omega$$

but since X_L cannot be negative

$$\therefore X_L = 4.038 \Omega$$

$$L = 0.0128 H$$

$$\tau = \sqrt{Z_{coil}^2 - X_L^2}$$

$$= \sqrt{(4.045)^2 - (4.038)^2}$$

$$\tau = 0.238 \Omega$$

Page No.:

Case II:- for (4 bulbs) - $\{V_s = 230.1V ; I_s = 3.05A\}$

1) Apparent Power = $V_s \times I_s = 230.1 \times 3.05 = \underline{701.805 VA}$

2) Power factor (ϕ) = $P/S = \underline{0.98}$

3) Total circuit Impedance (Z_s) = $V_s/I_s = \underline{75.44 \Omega}$

4) Total coil Impedance (Z_{coil}) = $V_{coil}/I_s = \underline{4.164 \Omega}$

5) Resistance of damp load (R) = $V_R/I_s = \underline{73.67 \Omega}$

6) Capacitive Reactance (X_c) = $V_c/I_s = \underline{16 \Omega}$

$X_L = ? \quad r = ?$

$Z_s^2 = (R+r)^2 + (X_L - X_c)^2 \text{ --- (i) ; } Z_{coil}^2 = r^2 + X_L^2 \text{ --- (ii)}$

solving (i) & (ii) simultaneously.

$Z_s^2 = (R + \sqrt{Z_{coil}^2 - X_L^2})^2 + (X_L - X_c)^2$

$Z_s^2 = R^2 + 2R(\sqrt{Z_{coil}^2 - X_L^2}) + Z_{coil}^2 - X_L^2 + X_L^2 - 2X_L X_c + X_c^2$

$Z_s^2 = R^2 + 2R(\sqrt{Z_{coil}^2 - X_L^2}) + Z_{coil}^2 - 2X_L X_c + X_c^2$

$5691.19 = 5427.27 + 147.34(\sqrt{17.34 - X_L^2}) + 17.34 - 32X_L$
 $+ 256$

$32X_L - 9.42 = 147.34(\sqrt{17.34 - X_L^2})$

$1024X_L^2 - 602.88X_L + 88.74 = 21709.08(17.34 - X_L^2)$

$\therefore 1024X_L^2 - 602.88X_L + 88.74 = 376435.45 - 21709.08X_L^2$

$\therefore 22733.08X_L^2 - 602.88X_L - 376346.71 = 0$

$X_L = \underline{4.083 \Omega}$

~~$r = 0.8$~~

$r = \underline{0.323 \Omega}$

$L = \underline{0.0129 H}$

$C = \underline{198.9 \mu F}$

Case III:- for (5 bulbs) - $\{V_s = 230.1V ; I_s = 3.81A\}$

1) Apparent Power = $V_s \times I_s = 230.1 \times 3.81 = \underline{876.681 VA}$

2) Power factor (ϕ) = $P/S = \underline{0.979}$

3) Total circuit Impedance (Z_s) = $V_s/I_s = \underline{60.393 \Omega}$

4) Total coil Impedance (Z_{coil}) = $V_{coil}/I_s = \underline{4.118 \Omega}$

5) Resistance of damp load (R) = $V_R/I_s = \underline{58.582 \Omega}$

6) Capacitive Reactance (X_c) = $V_c/I_s = \underline{15.958 \Omega}$

$X_L = ? \quad r = ?$

$Z_s^2 = (R+r)^2 + (X_L - X_c)^2 \text{ --- (i) ; } Z_{coil}^2 = r^2 + X_L^2 \text{ --- (ii)}$

solving (i) & (ii) simultaneously.

Page No. : _____

$$Z_s^2 = (R + \sqrt{Z_{coil}^2 - X_L^2})^2 + (X_L - X_C)^2$$

$$Z_s^2 = R^2 + 2R(\sqrt{Z_{coil}^2 - X_L^2}) + Z_{coil}^2 - X_L^2 + X_L^2 - 2X_L X_C + X_C^2$$

$$Z_s^2 = R^2 + 2R(\sqrt{Z_{coil}^2 - X_L^2}) + Z_{coil}^2 - 2X_L X_C + X_C^2$$

$$3647.314 = 3431.85 + 117.164(\sqrt{16.958 - X_L^2}) + 16.958 - 31.916X_L + 254.658$$

$$31.916X_L - 56.152 = 117.164(\sqrt{16.958 - X_L^2})$$

$$(31.916X_L - 56.152)^2 = 13727.4(16.958 - X_L^2)$$

$$1018.631X_L^2 - 3584.294X_L + 3153.047 = 232789.249 - 13727.4X_L^2$$

$$14746.031X_L^2 - 3584.294X_L - 229636.202 = 0$$


$$X_L = 4.069 \Omega$$

$$X_C = 0.233 \Omega$$


$$L = 0.0129 H$$

$$C = 199.46 \mu F$$


Phasor diagram ①

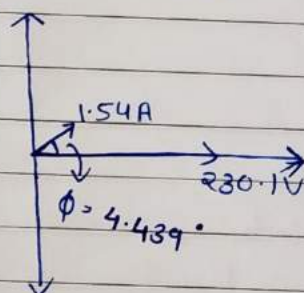

Phasor diagram (Case II)

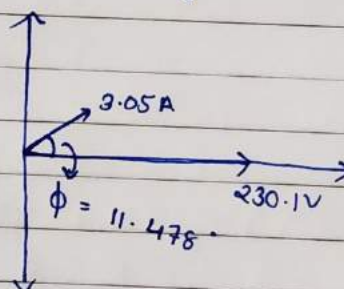

Phasor diagram (Case-III)

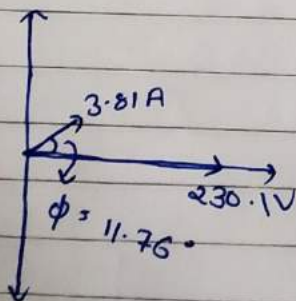

NAME: Pranay Singhvi EXPERIMENT No: 5

DATE: 5/7/ 2022

Measurement of power in R-L-C series circuit

AIM: 1) To obtain different types of power in R-L-C series circuit.

2) To verify the parameters used in the circuit with the help of the readings taken and vector diagram.

APPARATUS AND COMPONENTS REQUIRED:

Single phase auto-transformer (10A), Ammeter (0-10A), Wattmeter (10A/300V), Voltmeter (0-300V), Lamp-load, Inductors (12mH/10A), Capacitors (200 μ F), connecting wires.


THEORY: Write theory related with following questions:


- 1) Explain the behavior of series R-L-C circuit when single phase ac supplied is passed through it. Draw vector diagram for the same.

ANS: The series RLC circuit above has a single loop with the instantaneous current flowing through the loop being the same for each circuit element. Since the inductive and capacitive reactance's X_L and X_C are a function of the supply frequency, the sinusoidal response of a series RLC circuit will therefore vary with frequency, f . Then the individual voltage drops across each circuit element of R, L and C element will be "out-of-phase" with each other as defined by:

- $i(t) = I_{\max} \sin(\omega t)$
- The instantaneous voltage across a pure resistor, V_R is "in-phase" with current
- The instantaneous voltage across a pure inductor, V_L "leads" the current by 90°
- The instantaneous voltage across a pure capacitor, V_C "lags" the current by 90°
- Therefore, V_L and V_C are 180° "out-of-phase" and in opposition to each other.

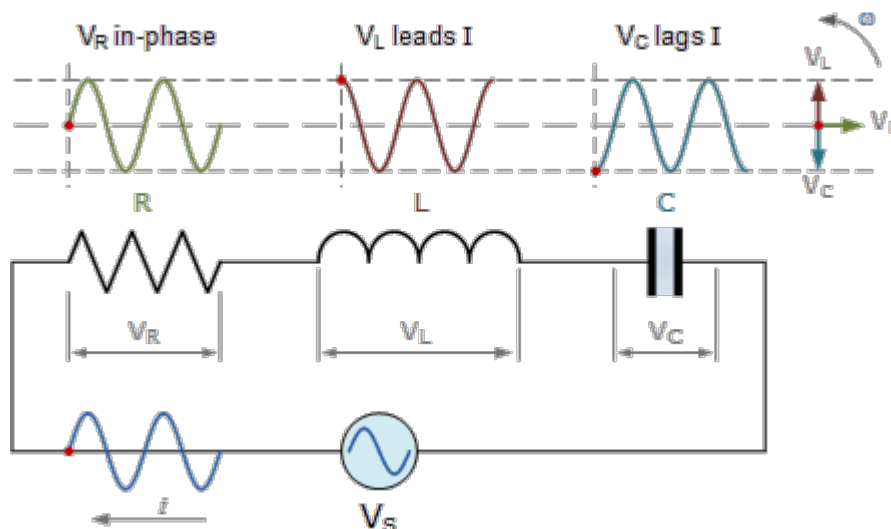For the series RLC circuit above, this can be shown as:



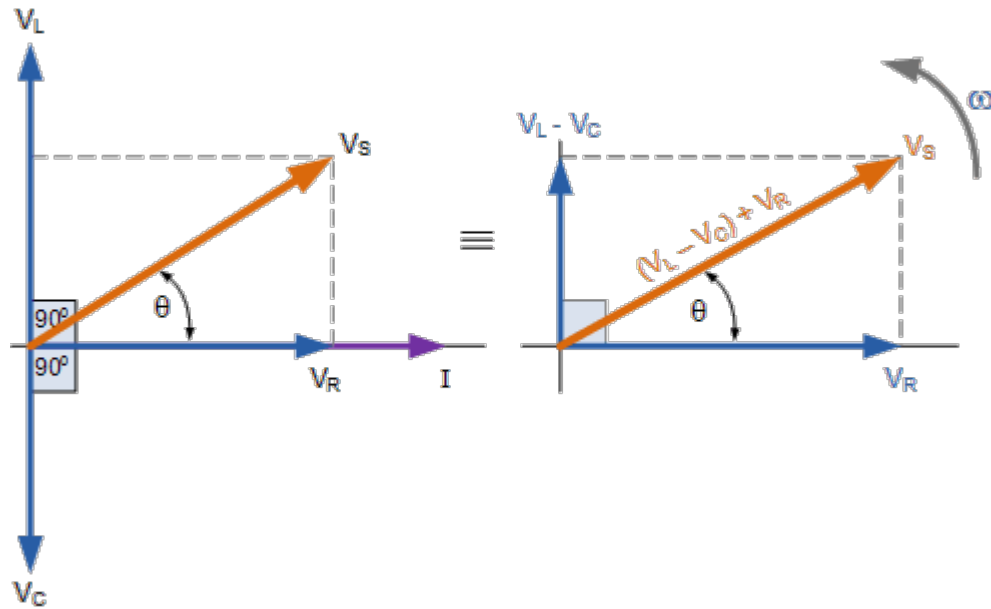

2) What is true, imaginary, and apparent power? Explain its significance.

ANS: 1. TRUE POWER: The actual amount of power being used, or dissipated, in a circuit is called *true power*, and it is measured in watts (symbolized by the capital letter P, as always).

2. IMAGINARY POWER: It is the part of complex power that corresponds to storage and retrieval of energy rather than consumption. Imaginary power provides the important function of regulating voltage.

3. APPARENT POWER: Apparent power is a measure of alternating current (AC) power that is computed by multiplying the root-mean-square (rms) current by the root-mean-square voltage. It is the apparent power seen to be consumed by the circuit.

PROCEDURE:

- 1) Connect the circuit as shown in the circuit diagram.
- 2) Adjust $V_S = 230$ V using auto transformer. Note down readings of ammeter (I_S) and wattmeter (P). Also measure V_R , V_L and V_C using multimeter.
- 3) Calculate apparent power S.
- 4) Obtain power factor from S and P.
- 5) Calculate resistance of lamp load R, resistance of coil r, reactance X_L and X_C .
- 6) Obtain L and C from X_L and X_C respectively.
- 7) Vary the load (Change the number of on bulbs).
- 8) Repeat steps 3) to 6).
- 9) Draw phasor diagram.

RESULT:

Parameter	R	r	L	C	P	Q	S	Power Factor
Is=1.54A	149.155ohm	0.238 ohm	12.8 millihenry	197.2 microfarad	353.4 W	25.984 VAR	354.354 VA	0.997
Is= 3.05A	73.67 ohm	0.322 ohm	12.9 millihenry	198.9 microfarad	673.3 W	197.983 VAR	701.805 VA	0.98
Is= 3.81A	58.582 ohm	0.233 ohm	12.9 millihenry	199.46 microfarad	858.3 W	178.579 VAR	876.681 VA	0.979

CONCLUSION:

From this experiment we learnt about series RLC circuit and what are the behaviours of the circuit connection to an AC source. We learnt about Real and Complex power and also the lagging and leading property of current in inductive and capacitive circuit respectively.