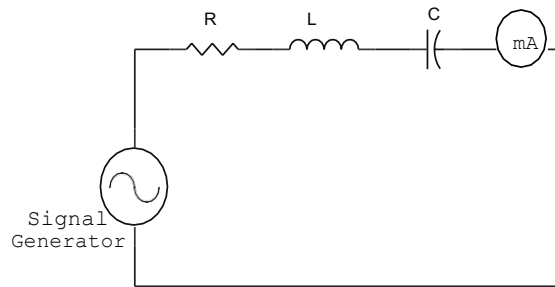


R-L-C Series Resonance

Name: Pranay Singhvi
UID: 2021300126
Batch: B4

CIRCUIT DIAGRAM:**OBSERVATION TABLE:**

,,

R=99.2 ohm, L= 0.1m henry, C=3.3microfarad**At Resonance frequency, $V_L=1.37V$; $V_C=1.37V$; $V=24.70mV$**

Sr. No.	Frequency (kHz)	Current (mA)
1	3	0.15
2	4	0.195
3	5	0.228
4	6	0.245
5	8.761	0.249
6	9	0.247
7	10	0.236
8	11	0.225
9	12	0.214
10	13	0.2

CALCULATIONS:

In an RLC series circuit impedance is given by $Z = \sqrt{R^2 + (X_L - X_C)^2}$. The frequency at which the power factor of the circuit is unity i.e. the reactive part in the impedance becomes zero is called resonant frequency. So, at resonance $X_L = X_C$ or $Z = R$.

$$\text{Hence, } 2\pi f_0 L = \frac{1}{2\pi f_0 C} \text{ or } f_0 = \frac{1}{2\pi\sqrt{LC}}$$

At resonance current is maximum ($=V/R$) whereas impedance Z is minimum ($=R$). Bandwidth of circuit is given by band of frequencies which lies between the two points at which the current is $1/\sqrt{2}$ times the current at resonant frequency.

$$\text{Bandwidth} = \frac{R}{2\pi L}$$

$$f_1 = f_0 - \frac{BW}{2} \text{ and } f_2 = f_0 + \frac{BW}{2}$$

The voltage magnification in series resonant circuit is expressed in terms of quality factor.

$$\text{Quality factor } Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$= (V_L \text{ or } V_C) / V$$

$$V_{\text{total}} = 24.70 \text{ mV} = V_R$$

$$V_L = 1.37 \text{ V} \quad V_C = 1.37 \text{ V}$$

$$\text{Bandwidth} = \frac{R}{2\pi L} = \frac{99.2 \times 10^3}{2 \times \pi \times 0.1} = 1.579 \times 10^3 \text{ Hz}$$

$$Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$= \frac{1}{99.2} \times \sqrt{\frac{0.1 \times 10^{-3}}{3.3 \times 10^{-6}}}$$

$$= \frac{1}{99.2} \times \sqrt{\frac{1}{33} \times 10^3}$$

$$\boxed{Q\text{-factor} = 0.055}$$

EXPERIMENT No: 6**DATE:- 19/07/ 2022****Resonance in RLC series circuit**


AIM: To verify resonance frequency, bandwidth and Q-factor of the given R-L-C series circuit.

APPARATUS AND COMPONENTS REQUIRED: Resistor (value), Inductor (value), Capacitor (Value), Signal Generator, Milliammeter, bread board, connecting wires, Sequel simulator

THEORY: Write theory related with following questions:

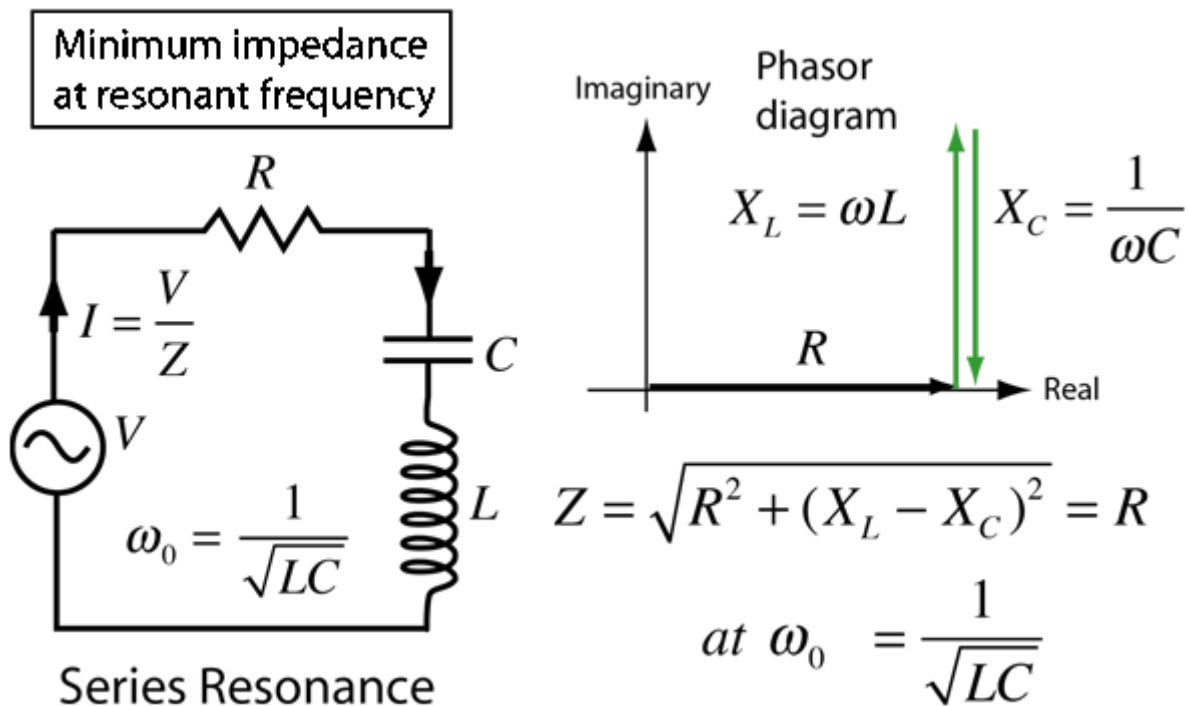1) What is resonance in R-L-C circuit and what is the condition to achieve it?

→ The resonance of a series RLC circuit occurs when the inductive and capacitive reactances are equal in magnitude but cancel each other because they are 180 degrees apart in phase. The sharp minimum in impedance which occurs is useful in tuning applications. The sharpness of the minimum depends on the value of R and is characterized by the "Q" of the circuit.



2) What is relation between bandwidth and selectivity factor.

→ The factor that affects both bandwidth and selectivity is known as Q (quality factor). The higher the Q, the better the filter; the lower the losses, the closer the filter is to being perfect. The Selectivity factor, Q of a series resonance circuit is the ratio of the center frequency to the bandwidth. $Q = f_c/BW$ so if the circuit has a narrow bandwidth its selectivity will be high, and if it has a wide bandwidth its selectivity will be low.

3) What is significance of Q-factor.

→ The Q factor implies energy losses within a resonant device that might be anything from a mechanical pendulum, an entity in a mechanical structure, or from an electrical circuit, such as a resonant circuit. Q factor shows the energy loss due to the quantity of energy contained in the design. Thus, the larger the Q factor, the lower the rate of energy loss, and hence the slower the oscillations.

4) List applications of resonance.

→ **1. Radio Transmissions and Television Broadcasts**

Most of us will experience using a resonant circuit as we attempt to tune into a radio frequency or pick up an analog television station. In doing so, we're adjusting the frequency so that the elements of the resonant circuit are in equilibrium. In the radio receiver, the tuning circuit is connected to the vehicle's antenna. The antenna receives electromagnetic waves of varying frequencies transmitted by different stations within a specific range. As you turn the dial, the frequencies generated in the antenna will have the same frequency as a local radio station. This means the tuning circuit in the radio receiver will only allow the current that has a matching frequency to that of the circuit to pass which in turn allows you to listen to a crystal-clear signal of your selected station.

2. Signal Processing and Communication Systems

Television and radio signals are an example of an application of resonance effect that many of us are most familiar with, but there are many other applications in which resonance circuits play an important role. Case in point: fiber optic data transmission. Fiber optics communication is used to transmit video, telemetry, and voice data all over the globe. Infrared light is sent through an optical cable, with the light carrying information—otherwise known as a carrier wave. The reason fiber is used instead of electrical cables is because it's immune to electromagnetic interference. It's also better at accommodating high bandwidth and longer distances.

3. Voltage Magnification

When the total circuit impedance is less than either the capacitive or inductive reactance at a resonant frequency, the supply voltage (developed across the circuit resistance) will be less than either of the opposing reactive voltages V_C or V_L . This effect, where the internal component reactive voltages are greater than the supply voltage is known as voltage magnification and there are several benefits associated with it. For example, when a circuit is configured in series, it can be used to magnify the voltage amplitude of a signal. When it comes to AC signal voltages, voltage magnification can be done passively, meaning the amplitude of the signal can be increased without a commensurate increase in power consumption. Voltage magnification is very useful and is most notably used in radio antennas. Radio receivers magnify the voltage amplitude of the signal voltage that is being received before it's fed to the transistor amplifiers in the circuit. Also, voltage magnification doesn't require an external power supply, making it even more beneficial.

4. Induction Heating

An induction heating system relies on access to a power supply, a circuit that contains matching impedance, a resonant circuit, and an applicator. In this instance, the resonant circuit is generally configured in parallel; within this circuit, the capacitors and inductors will store electrostatic and electromagnetic energy respectively. Once the circuit is at its resonant frequency, the elements will transfer power back and forth. Since the circuit is configured in parallel, this conversion will occur at a very high current. Energy is lost in the form of heat in the capacitor which results in the creation of induction heating. Induction heating is used within many industrial processes and is a quick way to heat metals. Technicians can use induction heating devices to create an electrical current in the metal object, generating heat. This is useful because then the metal becomes pliable

enough to be used for machining.

5. Oscillator Circuits

A crystal oscillator is an electronic oscillator circuit that is used to create an electrical signal with a given frequency. This frequency is commonly used to keep track of time and is used in a number of different timepieces. The crystal oscillator works in conjunction with a principle known as the inverse piezoelectric effect. Simply put, an electrical field produces a mechanical deformation within the crystal material. This deformation produces a vibration of the material's mechanical resonance to produce a very specific frequency. Common applications of oscillator circuits include alarms or buzzers within clocks or other devices. They can even be found in recreational or decorative products such as dance lights.

PROCEDURE:

- 1) Connect the Series RLC circuit as shown in circuit diagram.
- 2) Make sure that the milliammeter is in series with the circuit.
- 3) Keep the values fixed of R, L and C.
- 4) Keep varying frequency of the input signal from zero onwards
- 5) Measure frequency 'f' and current 'I' in mA.
- 6) Tabulate readings and draw graph of frequency v/s current.
- 7) Calculate value of bandwidth using formula $B.W = f_H - f_L$ from the graph.
- 8) Measure V_C or V_L and Supply voltage V at resonance to obtain Q as V_L/V
- 9) Implement the circuit using Sequel and verify answers of current, bandwidth and Q-factor using simulation.

RESULT TABLE:

Parameter	Theoretical	By Observation
f_0	8.761kHz	8.800 kHz
Bandwidth	1579Hz	1579Hz
Quality factor	0.5549	0.55

CONCLUSION:

In this experiment, I have learnt the R-L-C series resonance. I have seen how to find resonance frequency in the circuit and also find bandwidth through formula and also by graph and also the quality factor of the circuit.