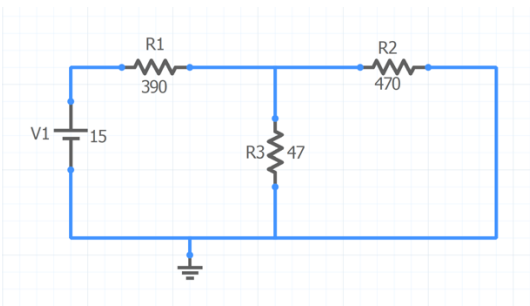
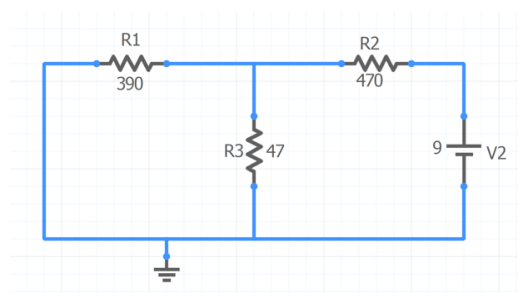
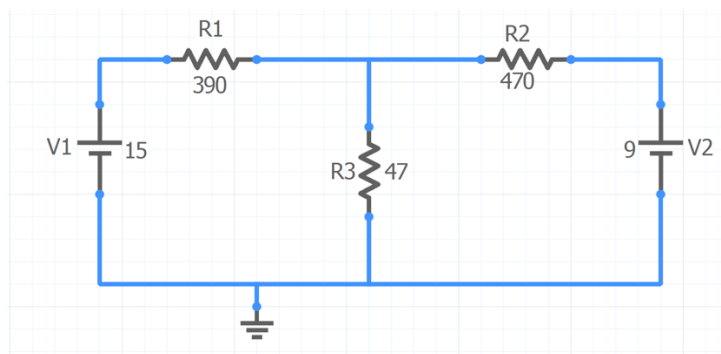


Verification of Superposition Theorem

Name: Pranay Singhvi

UID: 2021300126

Batch: B4

CIRCUIT DIAGRAM:**Figure 1****Figure 2****Figure 3****OBSERVATION TABLE:**

$R_1 = \underline{390\Omega}$, $R_2 = \underline{470\Omega}$, $R_3 = \underline{47\Omega}$

V_1 (V)	V_2 (V)	Current through R_1 (A)	Current through R_2 (A)	Current through R_3 (A)
15	-	$I_1' = 0.035$	$I_2' = 0.0032$	$I_3' = 0.032$
-	9	$I_1'' = 0.00189$	$I_2'' = 0.018$	$I_3'' = -0.0157$
15	9	$I_1 = 0.033$	$I_2 = 0.145$	$I_3 = 0.0477$

EXPERIMENT No: 2**DATE: / / 2022**

Verification of Superposition Theorem

AIM: To verify Superposition theorem using circuit implementation on breadboard and using simulator.

APPARATUS & COMPONENTS REQUIRED:

Resistors (values), Power supply(rating), DMM, connecting wires, breadboard, Sequel Simulator

THEORY: Write a theory related to the following questions.

- 1) Define linear, bilateral, and active elements.
Linear elements: Elements in which the constituent relation, the relation between voltage and current, is a linear function.
Bilateral elements: The elements through which the magnitude of the current is independent of the polarity of the supply voltage.
Active elements: An active element is an element capable of generating electrical energy
- 2) Write a statement of the Superposition theorem.
If more than one source acts simultaneously in an electric circuit, then the current through any one of the branches of the circuit is the summation of currents that would flow through that branch for each source acting alone, keeping all the other sources dead

PROCEDURE:

- 1) Connect the circuit as shown in the circuit diagram.
- 2) Apply voltage $V_1=15V$ and remove voltage V_2 and short the path.
- 3) Note down the current reading through R_1 , R_2 and R_3 due to voltage source $V_1=15V$.
- 4) Now remove V_1 and replace it by short path. Connect $V_2=9V$ and measure the current through R_1 , R_2 and R_3 due to $V_2=9V$.
- 5) Again, connect both the supply $V_1=15V$ and $V_2=9V$ and measure the current through R_1 , R_2 and R_3 .
- 6) Find the theoretical reading of current through R_1 , R_2 and R_3 using superposition theorem and verify it with the practical reading.
- 7) Repeat steps 2 to 6 by changing the voltage V_1 and V_2 .
- 8) Implement the given circuit using Sequel simulator.
- 9) Simulate the circuit, find currents, and verify them with theoretical values.

CALCULATION:

Step 1 :- Ignoring 9V source.

$$R_{eq} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} + R_1$$

$$R_{eq} = 432.73 \Omega$$

$$I_{Total} = \frac{15}{432.73} = 0.035 A$$

$I_1' = 0.0032$ (i) $I_2' = 0.035$ (ii) $I_3' = 0.032$ (iii)

Step 2 :- Ignoring 15V source


$$R_{eq} = \frac{R_1 R_3}{R_1 + R_3} + R_2$$

$$R_{eq} = 511.95 \Omega$$

$$I_{Total} = 0.0176 A$$


$I_1'' = -0.00189$ $I_2'' = -0.018$ $I_3'' = +0.0157$

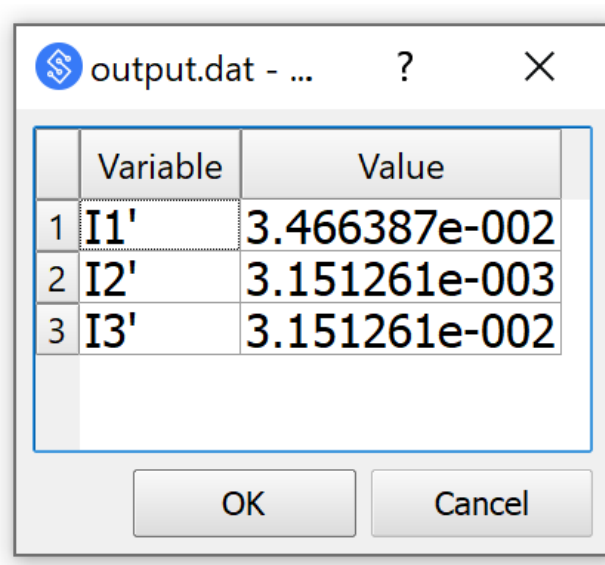$I_1 = I_1' + I_1'' = 0.035 + (-0.00189) = 0.0331 A$
 $I_2 = I_2' + I_2'' = 0.035 + (-0.018) = 0.017 A$
 $I_3 = I_3' + I_3'' = 0.032 + 0.0157 = 0.0477 A$




	Variable	Value
1	I1'	3.466387e-002
2	I2'	3.151261e-003
3	I3'	3.151261e-002

OK Cancel

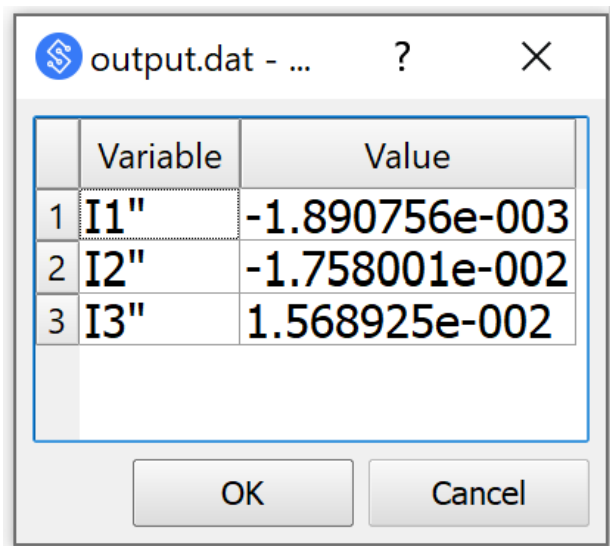

	Variable	Value
1	I1''	-1.890756e-003
2	I2''	-1.758001e-002
3	I3''	1.568925e-002

OK Cancel

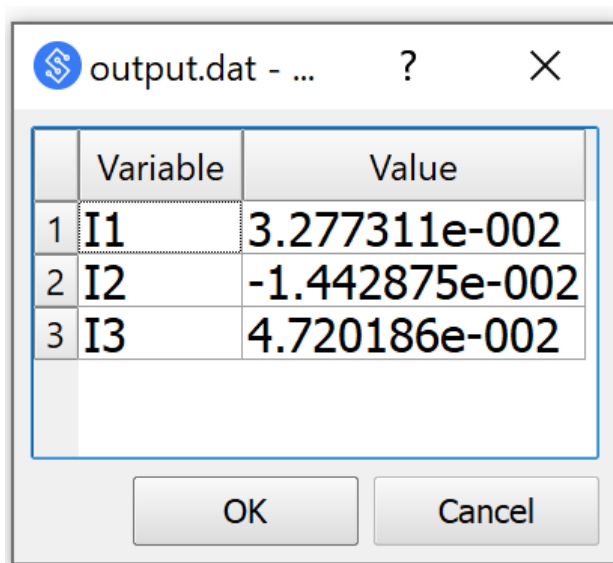

	Variable	Value
1	I1	3.277311e-002
2	I2	-1.442875e-002
3	I3	4.720186e-002

OK Cancel

RESULT TABLE

V₁ (V)	V₂ (V)	Current through R₁ (A)			Current through R₂ (A)			Current through R₃ (A)		
		Theoretical	Observed	By Simulation	Theoretical	Observed	By Simulation	Theoretical	Observed	By Simulation
15	-	0.035	0.035	0.0346	0.0032	0.0032	0.003151	0.032	0.032	0.03151
-	9	-0.00189	-0.00189	-0.00189	-0.018	-0.018	-0.0175	0.0157	0.0157	0.015689
15	9	0.0331	0.033	0.0327	-0.145	0.145	-0.1442	0.0477	0.0477	0.0472

CONCLUSION:

In this experiment, we learned about superposition theorem. We learned that we can calculate current across each resistor for each individual sources and then add them up to get net current across each resistor.